

CprE 381, Computer Organization and Assembly Level Programming

Lab 1 Report

Student Name: Jackson Hafele

[Part 1.c] Think of three more cases and record them in your lab report.

The following cases were used to test TPU_MV_Element in the file *tb_TPU_MV_Element.vhd*. The goal was to create test cases with varying weights iW, activation input iX, and partial sums iY.

iW	iX	iY	oX	oY
1000	5	25	5	5020
0	5	25	5	20
1	3	2	3	5

Table 1. tb_TPU_MV_Element Test Cases

[Part 1.e] For labels 1, 7, 22, and 28, specify where (VHDL file and line number) these values are located – some will be found in more than one place. Also attempt to explain the functionality of each label as it occurs in the code

In the attached diagram area, (1) is the top level TPU_MV_Element Module, which is defined in the TPU_MV_Element.vhd file. TPU_MV_Element is defined as an entity on line 19, and the components of TPU_MV_Element are defined starting at line 32.

In the attached diagram area, (7) is the g_Add1 module that is an Adder component. The Adder component is referenced on line 36 in the structure of TPU_MV_Element.vhd, and g_Add1 is instantiated on line 117, including the inputs iCLK, s_WxX, and s_Y1, and the output oY.

In the attached diagram area, (22) is the oQ output of the RegLd module, which is defined as an integer on Line 64 of TPU_MV_Element.vhd For this specific instance of the RegLd module, the output oQ is connected to a signal called s_W on line 86.

In the attached diagram area, (28) is the signal s_X1 wire in the TPU_MV_Element Module. s_X1 is defined as an integer on line 69. s_X1 is assigned as the output of oQ in the Module g_Delay1 on line 94 and as the input iD in the Module g_Delay3 on line 114.

[Part 1.g.v] In your lab report, include a screenshot of the waveform. Describe, in plain English, any differences between what you expected and what the simulation showed.

 


Figure 1. tb_TPU_MV_Element Waveform with bugs

Case 1 works as expected, but in case 2, after the activation input iX is loaded as 3 and the partial sum input iY is loaded as 25, the output should be $55 = 3 * 10 + 25$. Since the weight input iW is 10, it gets multiplied with iX and added to iY, for the partial sum output oY.

[Part 1.h] In your lab report, include a screenshot of the waveform. Describe, in plain English, how your waveform matches the expected result (e.g., reference the specific cycles and times). In your submission zip file, provide the completed TPU_MV_Element.vhd file in a folder called 'MAC'.

The error above was due to iX being assigned as the data input iD in the Reg module g_Delay2 instead of iY. Now, after two clock cycles, oY outputs as 55 as expected, and oX outputs the expected output 3.

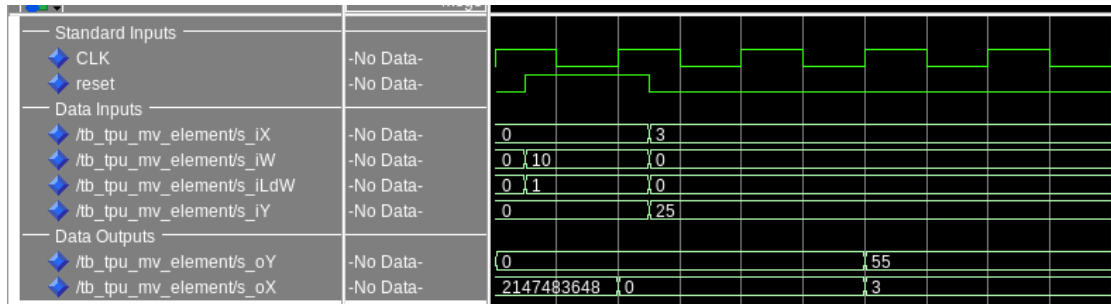


Figure 2. *tb_TPU_MV_Element Waveform After Debug*

I also updated tb_TPU_MV_Elements to include the three extra test cases listed in part 1c. After recompiling the testbench and running the .do file again, I verified that the expected results were met for oX and oY.

 


Figure 3. *tb_TPU_MV_Element Waveform With Additional Testcases*

[Part 3.a] Draw the truth table, Boolean equation, and Boolean circuit equivalent (using only two-input gates) that implements a 2:1 mux. Include this in your lab report.

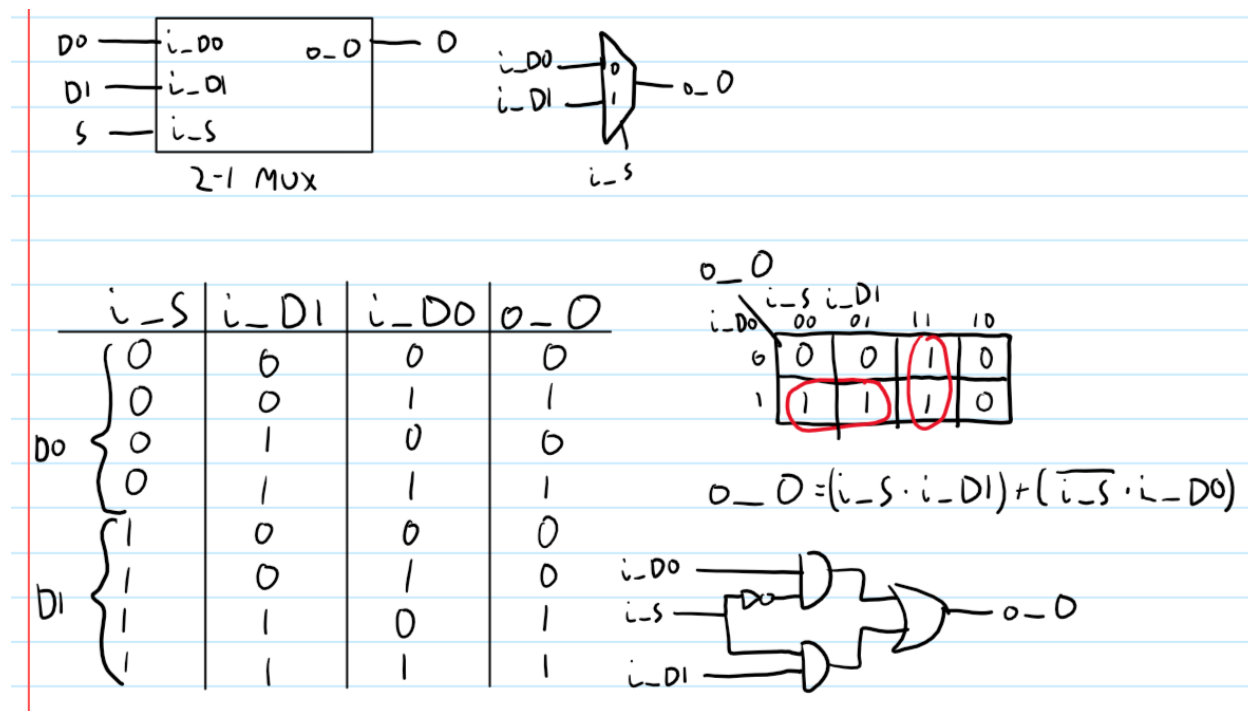


Figure 4. 2-1 MUX Block Diagram, Truth Table, K-Map, and Boolean Circuit

[Part 3.d] In your lab report, include a screenshot of the waveform. Make sure to label the screenshot with which module it is testing.

The testbench file I used to generate the waveform below was **tb_mux2t1**.

 


Figure 5. 2-1 mux2t1 Structural Waveform

[Part 3.e] Again, in your lab report, include a labeled screenshot of the waveform showing the dataflow mux implementation working.

The testbench file I used to generate the waveform below was **tb_mux2t1_behav**.

 


Figure 6. 2-1 mux2t1 Behavioral Waveform

By using the IEEE library for the 2 input AND and OR gates, along with the 1 input NOT gate, I was able to condense my code a ton. This is especially true since I did not have to include the component definitions of each gate before the begin statement in the architecture block.

[Part 4] Include a waveform screenshot and corresponding description demonstrating it is working correctly.

For this waveform design, I instantiated three different modules of mux2t1_n, named DUT0, DUT1, and DUT2, which contained N muxes for the generic values of 4, 8, and 16 respectively. I wanted to instantiate different sized modules so I could verify I had the correct syntax for the generic mapping. So, when DUT_select is 0, the outputs for DUT0 are checked, and so on for the other two DUT1/2 modules. I used one set of input pins and only used N bits needed for each DUT, to try and condense my waveforms. Because of this, the outputs for the other DUT's should not be used besides the one indicated by DUT_select for a given section. The testbench code used was in the file **tb_mux2t1_N**.

 


Figure 7. 2-1 mux2t1_N, DUT0 N=4 Waveform

 


Figure 8. 2-1 mux2t1_N, DUT1 N=8 Waveform



Figure 9. 2-1 mux2t1_N, DUT2 N=16 Waveform

As you can see in each waveform, the output o_O displays every bit of i_D0 when the select line i_S is 0, and outputs every bit of i_D1 when the select line i_S is 1.

[Part 5.b] Include a waveform screenshot and description in your lab report.

In this section, I created a testbench that was very similar to the mux2t1_N testing. s_i_A was my testbench signal to act as an N bit input for DUT0, DUT1, and DUT2, which were instances of the ones_comp module. The outputs s_o_F_DUT0, s_o_F_DUT1, and s_o_F_DUT2 were the outputs of the ones_comp modules, with respective integer inputs of 8, 16, and 32 bits. Since each DUT shared the same input s_i_A, I used the first 8 bits of that signal for DUT0, the first 16 bits for DUT1, and all 32 bits for DUT2. This helped me create a more concise testbench and compare results for the bits that were shared between each of the DUT modules.

 


Figure 10. ones_comp Waveform 1

 


Figure 11. ones_comp Waveform 2

[Part 6.a] A full adder takes three single-bit inputs and produces two single-bit outputs – a sum and carry for the addition of the three input bits. Draw the truth table, Boolean equation, and Boolean circuit equivalent (using only two-input gates) that implements a 1-bit full adder. Include this in your report.

Below, I derived the truth table, boolean equation, and boolean circuit equivalent for a 1 bit full adder circuit. I decided to take advantage of the fact that we were provided with a 2-input XOR gate to condense the structural design and circuit of the full adder

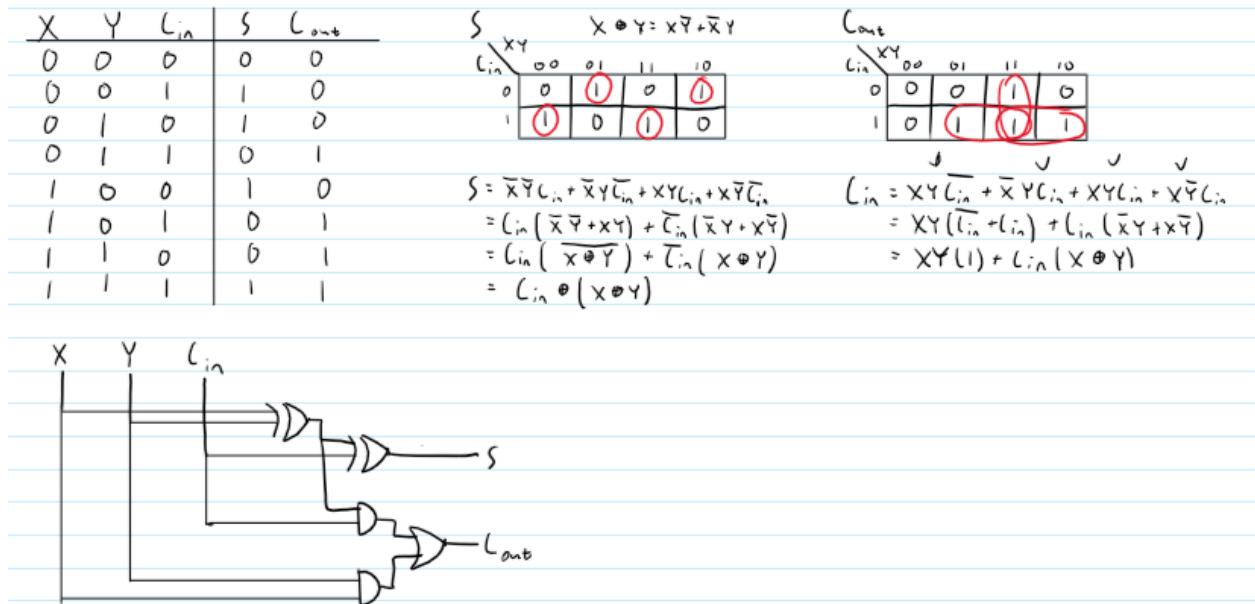


Figure 12. Full Adder Truth Table, K-Maps, Boolean Circuit

 


Figure 13. Full Adder Waveform

[Part 6.c] Then draw a schematic of the intended design, including inputs and outputs and at least the 0, 1, N-2, and N-1 stages. Include this in your report.

In this design, I routed the individual bit inputs for i_X and i_Y into the A and B inputs of each full_adder module. For each N bit ripple carry adder design, I planned to use N full_adder modules. The carryout bit of each full adder would get routed to the carry in bit of the next full adder.

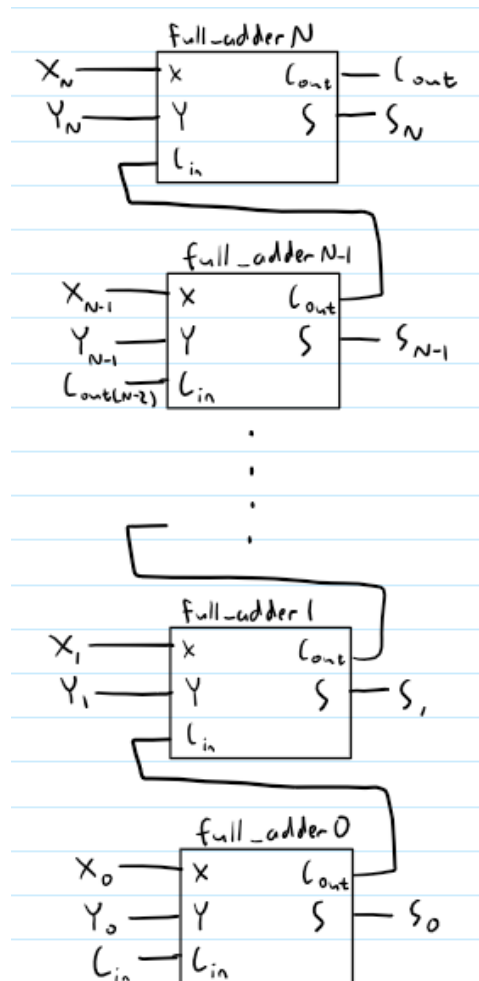


Figure 14. N-bit Ripple Carry Adder Block Diagram

[Part 6.d] Include an annotated waveform screenshot in your write-up.

Based on my waveforms below, I ran multiple different test cases to test my N bit ripple carry adder with a 16 bit component instantiated. I first decided to add together all three inputs, i_X, i_Y, and i_Cin as zero to verify both outputs o_S and o_Cout would return 0. After that, I tested adding just one input and the other two set to zero for all three inputs. After that, I tried together 0 and -1 to set o_Cout to 1. Then, I tried adding a very large negative signed value, along with some test cases similar to the TPU testbench in question 1c.

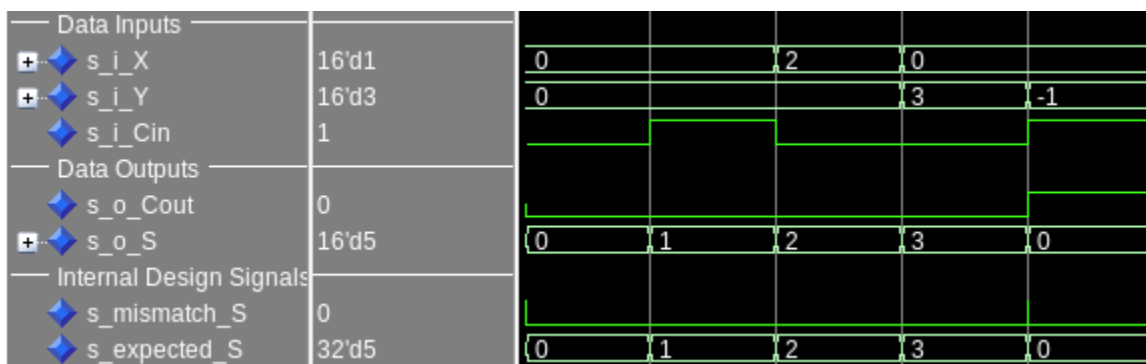


Figure 15. N-bit Ripple Carry Adder Waveform 1

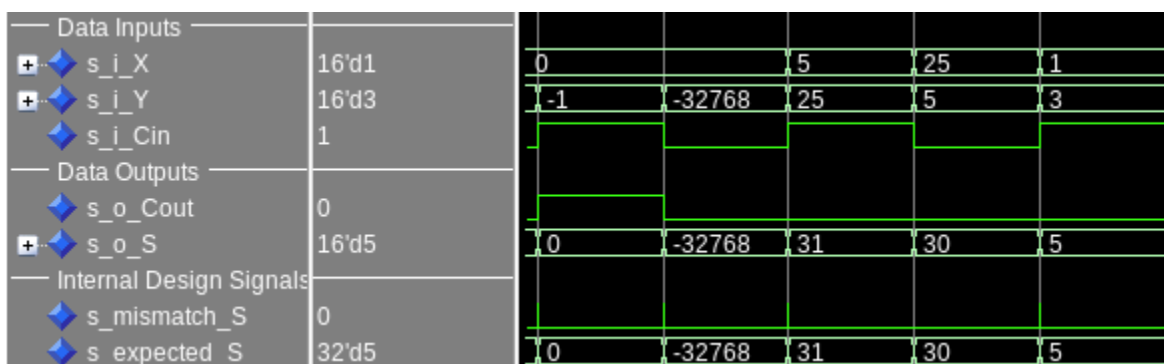


Figure 16. N-bit Ripple Carry Adder Waveform 2

Table 2 below shows the given test cases and expected results for the waveforms in **Figure 15** and **Figure 16** above.

i_X	i_Y	i_Cin	o_Cout	o_S	expected_S	expected_Cout
0	0	0	0	0	0	0
0	0	1	0	1	1	0
2	0	0	0	2	2	0
0	3	0	0	3	3	0
0	-1	1	1	0	0	1
0	-32768	0	0	-32768	-32768	0
5	31	1	0	31	31	0
25	30	0	0	30	30	0
1	5	1	0	5	5	0

Table 2. N-bit Ripple Carry Adder Test Cases

[Part 7.a] Draw a schematic (don't use a schematic capture tool) showing how an N-bit adder/subtractor with control can be implemented using only the three main components designed in earlier parts of this lab (i.e., the N-bit inverter, N-bit 2:1 mux, and N-bit adder). How is the 'nAdd_Sub' bit used? Include this in your report.

The design below incorporates the N-bit inverter, N-bit 2:1 mux, and the N-bit adder. Normally for an adder subtractor circuit, you use XOR gates with the B input and the nAdd_Sub control. Since we have to use the three modules we designed, we instead inverted all bits B with the N-bit inverter and used a multiplexer with nAdd_Sub as the select bit. If nAdd_Sub is 0, we are adding so the input B can be selected. If nAdd_Sub is 1, then B needs to be converted to two's complement, so the inverted B will be selected and the nAdd_Sub will be added as 1 for a carry in for the N-bit ripple carry adder module. Since we are controlling adding or subtracting B, we can just wire the input A to the ripple carry adder module. The output sum S is given for N bits after the ripple carry adder, along with a carryout.

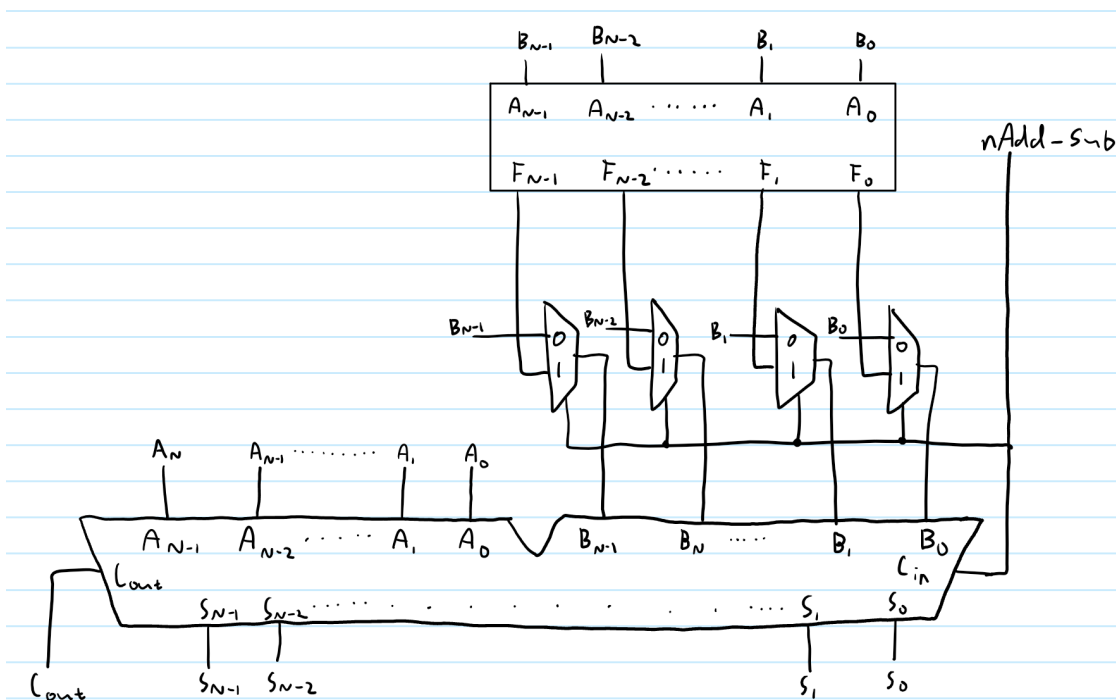


Figure 17. N-bit Adder Subtractor Block Diagram

[Part 7.c] Provide multiple waveform screenshots in your write-up to confirm that this component is working correctly. What test-cases did you include and why?

Below are the waveforms for the N-bit Adder Subtractor module. Waveform 1 describes when `i_nAdd_Sub` is 0, so the module is performing $A + B$. In Figure 19, Waveform 2 describes when `i_nAdd_Sub` is 1, where the module is performing the operation $A - B$.

My test cases were very similar for both the adding and subtracting cases. For adding, I first tried adding 0 for both inputs, to confirm my output would be 0. I then tried adding an individual value for both A and B to confirm they would be routed to the output. After that, I tried adding together two positive and two negative signed numbers. These operations were very similar for the second Waveform, except that the operation $A - B$ was being performed instead of $A + B$.

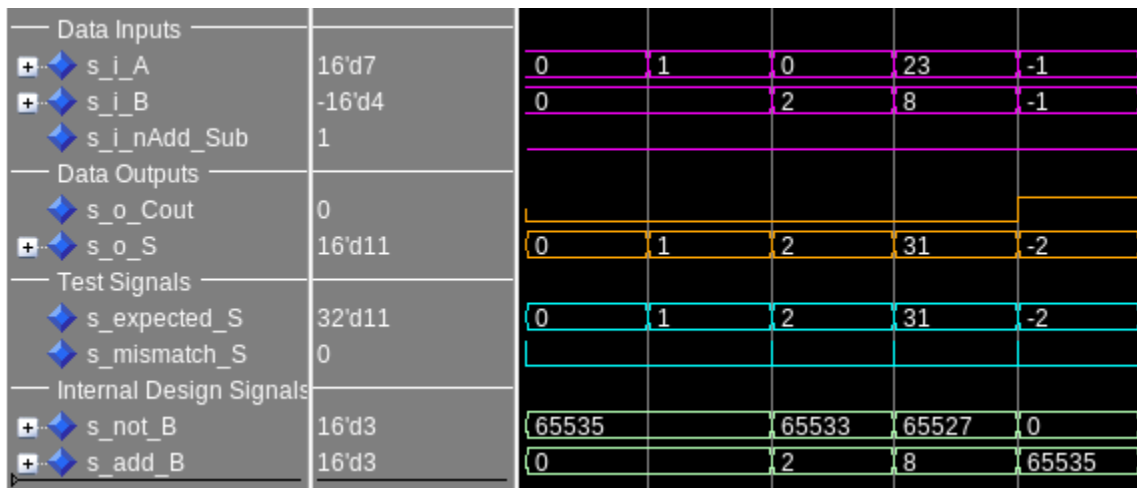


Figure 18. N-bit Adder Subtractor Waveform 1, `s_nAdd_Sub` = 0

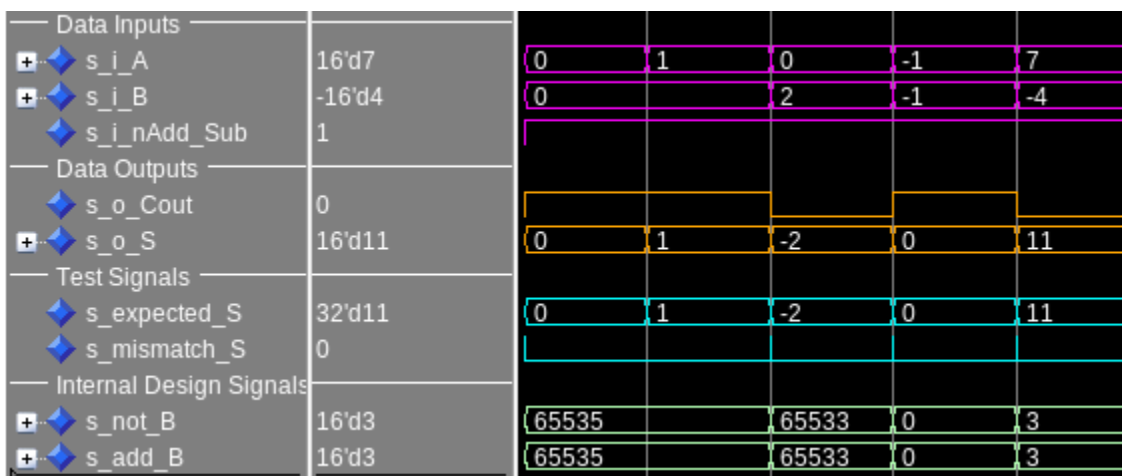


Figure 19. N-bit Adder Subtractor Waveform 2, `s_nAdd_Sub` = 1

Table 3 below shows the given test cases and expected results for the waveforms in **Figure 18** and **Figure 19** above.

i_X	i_Y	i_nAdd_Sub	o_Cout	o_S	expected_S	expected_Cout
0	0	0	0	0	0	0
1	0	0	0	1	1	0
0	2	0	0	2	2	0
23	8	0	0	31	31	0
-1	-1	0	1	-2	-2	1
0	0	1	1	0	0	1
1	0	1	1	1	1	1
0	2	1	0	-2	-2	0
-1	-1	1	1	0	0	1
7	-4	1	0	11	11	0

Table 3. N-bit Adder Subtractor Test Cases